





# Contadores Síncronos


Prof. Fernando Passold

Oct/2008, Abr/2020, 2022.

 
 
# Contador **síncrono** binario de 3 bits:




 
# Contador **síncrono** binario de 3 bits:



 
 
# Contador **síncrono** binario de 3 bits:



  
# Contador **síncrono** binario de 3 bits:



  
# Contador **síncrono** binario de 3 bits:



# Contador síncrono binário de 4 bits:

 

(a)

 

# Contador síncrono × assíncrono - Detalhes:

Contador **síncrono** 3 bits (módulo 8):


 


FIGURA 8.14 Contador binario síncrono de 3 bits.

 

Contador **assíncrono** 3 bits (módulo 8):


 


Figura 4.18

# Contador síncrono × assíncrono - Detalhes:

Contador **síncrono** 3 bits (módulo 8):

 


$$f_{MÁX} = \frac{1}{t_{P_{MÁX}}}$$

$$f_{MÁX} = \frac{1}{20 \times 10^{-9}}$$

$$f_{MÁX} = 50 \text{ MHz}$$

		Typ	Max	Min	Unit
$t_{PLH}$	Clock, Clear, Set to Output	15	20		ns
$t_{PHL}$					
$t_s$	Setup Time			20	ns
$t_h$	Hold Time			0	ns
$f_{max}$			45	30	MHz

 Contador **assíncrono** 3 bits (módulo 8):



$$f_{MÁX} = \frac{1}{2 \times t_{P_{MÁX}}}$$

$$f_{MÁX} = \frac{1}{40 \times 10^{-9}}$$

$$f_{MÁX} = 25 \text{ MHz}$$

# Contador síncrono × assíncrono - Detalhes:

- E sem problemas com *glitches*...

 


Figura acima: circuito de contador assíncrono com saídas decodificadas.

# Contador síncrono × assíncrono - Detalhes:

- E sem problemas com *glitches*...

 


Figura acima: circuito de contador assíncrono com saídas decodificadas.

# Contador síncrono × assíncrono - Detalhes:

- E sem problemas com *glitches*...


 



Figura acima: circuito de con

# Contador síncrono ascendente/descendente:

Contador síncrono creciente →

 


Comando bidireccional

 


# Contador síncrono ascendente/descendente (2):

*A four-bit synchronous "up" counter*

 


*A four-bit synchronous "down" counter*

 

# Contador síncrono ascendente/descendente (2):

A four-bit synchronous "up" counter

 

# CI's comerciais 74190/74191




- 74190: PRESETTABLE **BCD/DECADE** UP/DOWN COUNTERS
- 74191: PRESETTABLE **4-BIT BINARY** UP/DOWN COUNTERS

The SN54/74LS190 is a synchronous UP/DOWN BCD Decade (8421) Counter and the SN54/74LS191 is a synchronous UP/DOWN Modulo-16 Binary Counter. State changes of the counters are synchronous with the LOW-to-HIGH transition of the Clock Pulse input.

An asynchronous Parallel Load ( $\overline{PL}$ ) input overrides counting and loads the data present on the  $P_n$  inputs into the flip-flops, which makes it possible to use the circuits as programmable counters. A Count Enable ( $\overline{CE}$ ) input serves as the carry/borrow input in multi-stage counters. An Up/Down Count Control ( $\overline{U/D}$ ) input determines whether a circuit counts up or down. A Terminal Count ( $TC$ ) output and a Ripple Clock ( $\overline{RC}$ ) output provide overflow/underflow indication and make possible a variety of methods for generating carry/borrow signals in multistage counter applications.

 - Low Power ... 90 mW Typical Dissipation
- High Speed ... 25 MHz Typical Count Frequency
- Synchronous Counting
- Asynchronous Parallel Load
- Individual Preset Inputs
- Count Enable and Up/Down Control Inputs
- Cascadable
- Input Clamp Diodes Limit High Speed Termination Effects



$V_{CC} = \text{PIN } 16$   
 $GND = \text{PIN } 8$

$\overline{CE}$	Count Enable (Active LOW) Input
CP	Clock Pulse (Active HIGH going edge) Input
$\overline{U/D}$	Up/Down Count Control Input
$\overline{PL}$	Parallel Load Control (Active LOW) Input
$P_n$	Parallel Data Inputs
$Q_n$	Flip-Flop Outputs (Note b)
$\overline{RC}$	Ripple Clock Output (Note b)
TC	Terminal Count Output (Note b)

# CIs comerciais 74190/74191

## FUNCTIONAL DESCRIPTION

The LS190 is a synchronous Up/Down BCD Decade Counter and the LS191 is a synchronous Up/Down 4-Bit Binary Counter. The operating modes of the LS190 decade counter and the LS191 binary counter are identical, with the only difference being the count sequences as noted in the state diagrams. Each circuit contains four master/slave flip-flops, with internal gating and steering logic to provide individual preset, count-up and count-down operations.

Each circuit has an asynchronous parallel load capability permitting the counter to be preset to any desired number. When the Parallel Load ( $\overline{PL}$ ) input is LOW, information present on the Parallel Data inputs ( $P_0-P_3$ ) is loaded into the counter and appears on the Q outputs. This operation overrides the counting functions, as indicated in the Mode Select Table.

A HIGH signal on the  $\overline{CE}$  input inhibits counting. When  $\overline{CE}$  is LOW, internal state change are initiated synchronously by the LOW-to-HIGH transition of the clock input. The direction of counting is determined by the  $\overline{U/D}$  input signal, as indicated in the Mode Select Table. When counting is to be enabled, the  $\overline{CE}$  signal can be made LOW when the clock is in either state. However, when counting is to be inhibited, the LOW-to-HIGH  $\overline{CE}$  transition must occur only while the clock is HIGH. Similarly, the  $\overline{U/D}$  signal should only be changed when either  $\overline{CE}$  or the clock is HIGH.


Two types of outputs are provided as overflow/underflow indicators. The Terminal Count (TC) output is normally LOW and goes HIGH when a circuit reaches zero in the count-down mode or reaches maximum (9 for the LS190, 15 for the LS191) in the count-up mode. The TC output will then remain HIGH until a state change occurs, whether by counting or presetting or until  $\overline{U/D}$  is changed. The TC output should not be used as a clock signal because it is subject to decoding spikes.

The TC signal is also used internally to enable the Ripple

Clock ( $\overline{RC}$ ) output. The  $\overline{RC}$  output is normally HIGH. When  $\overline{CE}$  is LOW and TC is HIGH, the  $\overline{RC}$  output will go LOW when the clock next goes LOW and will stay LOW until the clock goes HIGH again. This feature simplifies the design of multi-stage counters, as indicated in Figures a and b. In Figure a, each  $\overline{RC}$  output is used as the clock input for the next higher stage. This configuration is particularly advantageous when the clock source has a limited drive capability, since it drives only the first stage. To prevent counting in all stages it is only necessary to inhibit the first stage, since a HIGH signal on  $\overline{CE}$  inhibits the  $\overline{RC}$  output pulse, as indicated in the  $\overline{RC}$  Truth Table. A disadvantage of this configuration, in some applications, is the timing skew between state changes in the first and last stages. This represents the cumulative delay of the clock as it ripples through the preceding stages.

A method of causing state changes to occur simultaneously in all stages is shown in Figure b. All clock inputs are driven in parallel and the  $\overline{RC}$  outputs propagate the carry/borrow signals in ripple fashion. In this configuration the LOW state duration of the clock must be long enough to allow the negative-going edge of the carry/borrow signal to ripple through to the last stop before the clock goes HIGH. There is no such restriction on the HIGH state duration of the clock, since the  $\overline{RC}$  output of any package goes HIGH shortly after its CP input goes HIGH.

The configuration shown in Figure c avoids ripple delays and their associated restrictions. The  $\overline{CE}$  input signal for a given stage is formed by combining the TC signals from all the preceding stages. Note that in order to inhibit counting an enable signal must be included in each carry gate. The simple inhibit scheme of Figures a and b doesn't apply, because the TC output of a given stage is not affected by its own  $\overline{CE}$ .

 

MODE SELECT TABLE

INPUTS				MODE
PL	CE	$\overline{U/D}$	CP	
H	L	L	$\downarrow$	Count Up
H	L	H	$\downarrow$	Count Down
L	X	X	X	Preset (Asyn.)
H	H	X	X	No Change (Hold)

RC TRUTH TABLE



INPUTS			RC OUTPUT
$\overline{CE}$	TC*	CP	
L	H	$\downarrow$	$\downarrow$
H	X	X	H
X	L	X	H

\* TC is generated internally

- L = LOW Voltage Level
- H = HIGH Voltage Level
- X = Don't Care
- $\downarrow$  = LOW-to-HIGH Clock Transition
- $\downarrow$  = LOW Pulse
  
# CIs comerciais 74190/74191

Detalhe do "Parallel Load" ( $\overline{PL}$ ):



VCC = PIN 16  
GND = PIN 8

MODE SELECT TABLE

INPUTS				MODE
PL	CE	$\overline{U/D}$	CP	
H	L	L	$\uparrow$	Count Up
H	L	H	$\uparrow$	Count Down
L	X	X	X	Preset (Asyn.)
H	H	X	X	No Change (Hold)

RC TRUTH TABLE

INPUTS			RC OUTPUT
CE	TC*	CP	
L	H	$\square$	$\square$
H	X	X	H
X	L	X	H

\* TC is generated internally

- L = LOW Voltage Level
- H = HIGH Voltage Level
- X = Don't Care
- $\uparrow$  = LOW-to-HIGH Clock Transition
- $\square$  = LOW Pulse


# CIs comerciais 74190/74191

Tabelas funcionais...

- 74190: PRESETTABLE BCD/DECADE UP/DOWN COUNTERS
- 74191: PRESETTABLE 4-BIT BINARY UP/DOWN COUNTERS



 The SN54/74LS190 is a synchronous UP/DOWN BCD Decade (8421 Counter) and the SN54/74LS191 is a synchronous UP/DOWN Modulo-16 Binary Counter. State changes of the counters are synchronous with the clock.



- $\overline{CE}$  Count Enable (Active LOW) Input
- CP Clock Pulse (Active HIGH going edge) Input
- $\overline{U/D}$  Up/Down Count Control Input
- $\overline{PL}$  Parallel Load Control (Active LOW) Input
- $P_n$  Parallel Data Inputs
- $Q_n$  Flip-Flop Outputs (Note b)
- $\overline{RC}$  Ripple Clock Output (Note b)
- TC Terminal Count Output (Note b)

## $\overline{RC}$ Truth Table

Inputs			Output
$\overline{CE}$	TC*	CP	$\overline{RC}$
L	H	$\downarrow$	$\downarrow$
H	X	X	H
X	L	X	H

## Mode Select Table

Inputs				Mode
$\overline{PL}$	$\overline{CE}$	$\overline{U/D}$	CP	
H	L	L	$\nearrow$	Count Up
H	L	H	$\nearrow$	Count Down
L	X	X	X	Preset (Asyn.)
H	H	X	X	No Change (Hold)

\*TC is generated internally

H = HIGH Voltage Level


L = LOW Voltage Level

X = Immaterial

$\nearrow$  = LOW-to-HIGH Clock Transition

$\downarrow$  = LOW Pulse


# CIs comerciais 74190/74191

 

$V_{CC} = \text{PIN } 16$   
 $GND = \text{PIN } 8$

- $\overline{CE}$  Count Enable (Active LOW) Input
- CP Clock Pulse (Active HIGH going edge) Input
- $\overline{U/D}$  Up/Down Count Control Input
- $\overline{PL}$  Parallel Load Control (Active LOW) Input
- $P_n$  Parallel Data Inputs
- $Q_n$  Flip-Flop Outputs (Note b)
- $\overline{RC}$  Ripple Clock Output (Note b)
- TC Terminal Count Output (Note b)

## STATE DIAGRAMS

 

LS190

**LS190**  
 UP:  $TC = Q_0 \cdot Q_3 \cdot (\overline{U/D})$   
 DOWN:  $TC = Q_0 \cdot Q_1 \cdot Q_2 \cdot Q_3 \cdot (\overline{U/D})$


**LS191**  
 UP:  $TC = Q_0 \cdot Q_1 \cdot Q_2 \cdot Q_3 \cdot (\overline{U/D})$   
 DOWN:  $TC = Q_0 \cdot Q_1 \cdot Q_2 \cdot Q_3 \cdot (\overline{U/D})$

COUNT UP ———  
 COUNT DOWN - - - -



LS191

## LOGIC DIAGRAMS

 


$V_{CC} = \text{PIN } 16$   
 $GND = \text{PIN } 8$


○ = PIN NUMBERS

**DECADE COUNTER**  
**LS190**

# CIs comerciais 74190/74191

 

STATE DIAGRAMS

 


LS190

**LS190**  
 UP:  $TC = Q_0 \cdot Q_3 \cdot (U/D)$   
 DOWN:  $TC = Q_0 \cdot \overline{Q_1} \cdot Q_2 \cdot Q_3 \cdot (U/D)$

**LS191**  
 UP:  $TC = Q_0 \cdot Q_1 \cdot Q_2 \cdot Q_3 \cdot (U/D)$   
 DOWN:  $TC = \overline{Q_0} \cdot \overline{Q_1} \cdot \overline{Q_2} \cdot \overline{Q_3} \cdot (U/D)$

COUNT UP ———  
 COUNT DOWN - - - -

 


LS191

LOGIC DIAGRAMS

## Diagrama de Estados

VCC  
 GND

$\overline{CE}$  Count Enable  
 $\overline{CP}$  Clock Pulse (A)  
 $\overline{U/D}$  Up/Down Counting  
 $\overline{PL}$  Parallel Load  
 $P_n$  Parallel Data  
 $Q_n$  Flip-Flop Output  
 $\overline{RC}$  Ripple Clock Output  
 $\overline{TC}$  Terminal Count

 


LS190

**LS190**  
 UP:  $TC = Q_0 \cdot Q_3 \cdot (U/D)$   
 DOWN:  $TC = Q_0 \cdot \overline{Q_1} \cdot Q_2 \cdot Q_3 \cdot (U/D)$

**LS191**  
 UP:  $TC = Q_0 \cdot Q_1 \cdot Q_2 \cdot Q_3 \cdot (U/D)$   
 DOWN:  $TC = \overline{Q_0} \cdot \overline{Q_1} \cdot \overline{Q_2} \cdot \overline{Q_3} \cdot (U/D)$

COUNT UP ———  
 COUNT DOWN - - - -

 


LS191

VCC = PIN 16  
 GND = PIN 8  
 ○ = PIN NUMBERS


DECADE COUNTER  
**LS190**

# CIs comerciales 74190/74191

 

VCC = PIN 16  
GND = PIN 8


## Diagrama lógico

 



**DECADE COUNTER  
LS190**

VCC = PIN 16  
GND = PIN 8  
○ = PIN NUMBERS


# Exemplo de uso de 74190

 

Crescente:  
[0..9]

 
 


 - $\overline{CE}$  Count Enable (Active LOW) Input
- CP Clock Pulse (Active HIGH going edge) Input
- $\overline{U/D}$  Up/Down Count Control Input
- $\overline{PL}$  Parallel Load Control (Active LOW) Input
- $P_n$  Parallel Data Inputs
- $Q_n$  Flip-Flop Outputs (Note b)
- RC Ripple Clock Output (Note b)
- TC Terminal Count Output (Note b)



# Exemplo de uso de 74190

Decrescente:  
[9..0]

  


- $\overline{CE}$  Count Enable (Active LOW) Input
- CP Clock Pulse (Active HIGH going edge) Input
- $\overline{U/D}$  Up/Down Count Control Input
- $\overline{PL}$  Parallel Load Control (Active LOW) Input
- $P_n$  Parallel Data Inputs
- $Q_n$  Flip-Flop Outputs (Note b)
- $\overline{RC}$  Ripple Clock Output (Note b)
- TC Terminal Count Output (Note b)

# CIs comerciais 74190/74191

Características AC:

$\overline{CE}$   
 $\overline{CP}$   
 $\overline{U/D}$   
 $\overline{PL}$   
 $P_n$   
 $Q_n$   
 $\overline{RC}$   
 $\overline{TC}$

 **Count Enable (Active LOW) Input**  
**Clock Pulse (Active HIGH going edge)**  
**Up/Down Count Control Input**  
**Parallel Load Control (Active LOW) Inp**  
**Parallel Data Inputs**  
**Flip-Flop Outputs (Note b)**  
**Ripple Clock Output (Note b)**  
**Terminal Count Output (Note b)**



## AC CHARACTERISTICS ( $T_A = 25^\circ\text{C}$ )

Symbol	Parameter	Limits			Unit	Test Conditions
		Min	Typ	Max		
$f_{\text{MAX}}$	Maximum Clock Frequency	20	25		MHz	$V_{CC} = 5.0 \text{ V}$ $C_L = 15 \text{ pF}$
$t_{\text{PLH}}$ $t_{\text{PHL}}$	Propagation Delay, PL to Output Q		22 33	33 50	ns	
$t_{\text{PLH}}$ $t_{\text{PHL}}$	Data to Output Q		20 27	32 40	ns	
$t_{\text{PLH}}$ $t_{\text{PHL}}$	Clock to $\overline{RC}$		13 16	20 24	ns	
$t_{\text{PLH}}$ $t_{\text{PHL}}$	Clock to Output Q		16 24	24 36	ns	
$t_{\text{PLH}}$ $t_{\text{PHL}}$	Clock to TC		28 37	42 52	ns	
$t_{\text{PLH}}$ $t_{\text{PHL}}$	$\overline{U/D}$ to $\overline{RC}$		30 30	45 45	ns	
$t_{\text{PLH}}$ $t_{\text{PHL}}$	$\overline{U/D}$ to TC		21 22	33 33	ns	
$t_{\text{PLH}}$ $t_{\text{PHL}}$	$\overline{CE}$ to $\overline{RC}$		21 22	33 33	ns	

## AC SETUP REQUIREMENTS ( $T_A = 25^\circ\text{C}$ )

Symbol	Parameter	Limits			Unit	Test Conditions
		Min	Typ	Max		
$t_W$	CP Pulse Width	25			ns	$V_{CC} = 5.0 \text{ V}$
$t_W$	$\overline{PL}$ Pulse Width	35			ns	
$t_s$	Data Setup Time	20			ns	
$t_h$	Data Hold Time	5.0			ns	
$t_{\text{rec}}$	Recovery Time	40			ns	

## DEFINITIONS OF TERMS

**SETUP TIME ( $t_s$ )** is defined as the minimum time required for the correct logic level to be present at the logic input prior to the clock transition from LOW-to-HIGH in order to be recognized and transferred to the outputs.


**HOLD TIME ( $t_h$ )** is defined as the minimum time following the clock transition from LOW-to-HIGH that the logic level must be maintained at the input in order to ensure continued recogni-

tion. A negative HOLD TIME indicates that the correct logic level may be released prior to the clock transition from LOW-to-HIGH and still be recognized.

**RECOVERY TIME ( $t_{\text{rec}}$ )** is defined as the minimum time required between the end of the reset pulse and the clock transition from LOW-to-HIGH in order to recognize and transfer HIGH data to the Q outputs.
 
# CIs comerciais 74190/74191

- $\overline{CE}$  Count Enable (Active LOW) Input
- CP Clock Pulse (Active HIGH going edge) Input
- $\overline{U/D}$  Up/Down Count Control Input
- $\overline{PL}$  Parallel Load Control (Active LOW) Input
- $P_n$  Parallel Data Inputs
- $Q_n$  Flip-Flop Outputs (Note b)
- RC Ripple Clock Output (Note b)
- TC Terminal Count Output (Note b)



Opções de cascadeamento:

## LS190

- UP:  $TC = Q_0 \cdot Q_3 \cdot (\overline{U/D})$
- DOWN:  $TC = Q_0 \cdot Q_1 \cdot Q_2 \cdot Q_3 \cdot (\overline{U/D})$

## SN54/74LS190 • SN54/74LS191

 


Figure a. n-Stage Counter Using Ripple Clock

 


Figure b. Synchronous n-Stage Counter Using Ripple Carry/Borrow

 


Figure c. Synchronous n-Stage Counter with Parallel Gated Carry/Borrow

# 74190:

## Opções de cascadeamento:

 
 
 


Figure a. n-Stage Counter Using Ripple Clock

 


Figure b. Synchronous n-Stage Counter Using Ripple Carry/Borrow



 
 


Figure c. Synchronous n-Stage Counter with Parallel Gated Carry/Borrow

 


# Usando entradas PL num 74190


 


Repare:  
Pin  $\overline{RCO}$  → pin  $\overline{PL}$

 Sequência assumida:  
0 → 1 → 2 → 3 → 4 → 5 → 6 → 8 → 9/5 →  
→ 6 → 7 → 8 → 9/5 → 6 → 7 → 8 → ...




# Ex.2: Contador decrescente de 5 → 1:

  


Repare:  
 $\overline{PL} = \overline{TC}$   
 $P_3P_2P_1P_0 = 0101_{(2)} = 5_{(10)}$   
 $D/\overline{U} = 1$

 Sequência assumida:  
 5 → 4 → 3 → 2 → 1 → 0/5 → 4 → 3 → 2 →  
 → 1 → 0/5 → 4 → 3 → 2 → 1 → ...



# Ex.3: Contador decrescente de 5 → 1:

Simulado à frequência de 5 MHz

 

Repare:


$$\overline{PL} \leftarrow \overline{RCO}$$

$$P_3P_2P_1P_0 = 0101_{(2)} = 5_{(10)}$$

$$D/\overline{U} = 1$$

Sequência assumida:

 5 → 4 → 3 → 2 → 1 → 0/5 → 4 → 3 → 2 →  
→ 1 → 0/5 → 4 → 3 → 2 → 1 → ...




Desejado:  $PL = \overline{INIT} + \overline{RCO}$

Deve-se gerar  $\overline{PL}$  :


$$\overline{PL} = \overline{\overline{INIT} + \overline{RCO}}$$

Mas disponíveis:  $\overline{\overline{INIT}}$ ,  $\overline{\overline{RCO}}$  :


 
$$\overline{PL} = \overline{\overline{\overline{INIT} + \overline{RCO}}}$$


 
# Ex.4: Divisor de frequência, $f \div 8$ :



Simulado à frequência de 80 KHz

  

# Pastilhas 74192/74193:




## PRESETTABLE BCD/DECADE UP/DOWN COUNTER

## PRESETTABLE 4-BIT BINARY UP/DOWN COUNTER

The SN54/74LS192 is an UP/DOWN BCD Decade (8421) Counter and the SN54/74LS193 is an UP/DOWN MODULO-16 Binary Counter. Separate Count Up and Count Down Clocks are used and in either counting mode the circuits operate synchronously. The outputs change state synchronous with the LOW-to-HIGH transitions on the clock inputs.

Separate Terminal Count Up and Terminal Count Down outputs are provided which are used as the clocks for a subsequent stages without extra logic, thus simplifying multistage counter designs. Individual preset inputs allow the circuits to be used as programmable counters. Both the Parallel Load ( $\overline{PL}$ ) and the Master Reset (MR) inputs asynchronously override the clocks.

 - Low Power . . . 95 mW Typical Dissipation
- High Speed . . . 40 MHz Typical Count Frequency
- Synchronous Counting
- Asynchronous Master Reset and Parallel Load
- Individual Preset Inputs
- Cascading Circuitry Internally Provided
- Input Clamp Diodes Limit High Speed Termination Effects



- CPU Count Up Clock Pulse Input
- CPD Count Down Clock Pulse Input
- MR Asynchronous Master Reset (Clear) Input
- $\overline{PL}$  Asynchronous Parallel Load (Active LOW) Input
- $P_n$  Parallel Data Inputs
- $Q_n$  Flip-Flop Outputs (Note b)
- TCD Terminal Count Down (Borrow) Output (Note b)
- TCU Terminal Count Up (Carry) Output (Note b)

**NOTES:**

- a. 1 TTL Unit Load (U.L.) = 40  $\mu$ A HIGH/1.6 mA LOW.
- b. The Output LOW drive



**MODE SELECT TABLE**

MR	$\overline{PL}$	CPU	CPD	MODE
H	X	X	X	Reset (Asyn.)
L	L	X	X	Preset (Asyn.)
L	H	H	H	No Change
L	H	$\downarrow$	H	Count Up
L	H	H	$\downarrow$	Count Down

- L = LOW Voltage Level
- H = HIGH Voltage Level
- X = Don't Care
- $\downarrow$  = LOW-to-HIGH Clock Transition

# Pastilhas 74192/74193:

## LOGIC DIAGRAMS

  

VCC = PIN 16  
GND = PIN 8  
○ = PIN NUMBERS

- CPU Count Up Clock Pulse Input
- CPD Count Down Clock Pulse Input
- MR Asynchronous Master Reset (Clear) Input
- PL Asynchronous Parallel Load (Active LOW) Input
- P<sub>n</sub> Parallel Data Inputs
- Q<sub>n</sub> Flip-Flop Outputs (Note b)
- TCD Terminal Count Down (Borrow) Output (Note b)
- TCU Terminal Count Up (Carry) Output (Note b)

**NOTES:**

- a. 1 TTL Unit Load (U.L.) = 40 μA HIGH/1.6 mA LOW.
- b. The Output LOW drive


**MODE SELECT TABLE**

MR	PL	CPU	CPD	MODE
H	X	X	X	Reset (Asyn.)
L	L	X	X	Preset (Asyn.)
L	H	H	H	No Change
L	H	⌋	H	Count Up
L	H	H	⌋	Count Down

L = LOW Voltage Level  
H = HIGH Voltage Level  
X = Don't Care  
⌋ = LOW-to-HIGH Clock Transition

 
# Pastilhas comerciais:

- Contador síncrono up/down: 74HC192/74HC193




**CP<sub>U</sub>** Count Up Clock Pulse Input  
**CP<sub>D</sub>** Count Down Clock Pulse Input  
**MR** Asynchronous Master Reset (Clear) Input  
**PL** Asynchronous Parallel Load (Active LOW) Input  
**P<sub>n</sub>** Parallel Data Inputs  
**Q<sub>n</sub>** Flip-Flop Outputs (Note b)  
**T<sub>C</sub>D** Terminal Count Down (Borrow) Output (Note b)  
**T<sub>C</sub>U** Terminal Count Up (Carry) Output (Note b)

 **NOTES:**  
 a. 1 TTL Unit Load (U.L.) = 40 μA HIGH/1.6 mA LOW.  
 b. The Output LOW drive



**V<sub>CC</sub> = PIN 16**  
**GND = PIN 8**

## STATE DIAGRAMS

 

**LS192**

## LS192 LOGIC EQUATIONS FOR TERMINAL COUNT

$$\overline{TC}_U = Q_0 \cdot Q_3 \cdot \overline{CP}_U$$


$$\overline{TC}_D = Q_0 \cdot Q_1 \cdot Q_2 \cdot Q_3 \cdot \overline{CP}_D$$

## LS193 LOGIC EQUATIONS FOR TERMINAL COUNT

$$\overline{TC}_U = Q_0 \cdot Q_1 \cdot Q_2 \cdot Q_3 \cdot \overline{CP}_U$$

$$\overline{TC}_D = Q_0 \cdot Q_1 \cdot Q_2 \cdot Q_3 \cdot \overline{CP}_D$$


**COUNT UP** ———  
**COUNT DOWN** - - - -

 

**LS193**
 
# Usando o CI 74193:


Complete as formas de onda nas saídas do 74193:



# Usando o CI 74192:

Que acontece quando ?

 - 1) Resseto todas as suas saídas;
- 2) Realizo carga paralela com  $7(10)=0111(2)$ ;
- 3) Ajusto para contar crescente +5 pulsos de Clock;
- 4) Ajusto para contar decrescente + 5 pulsos de




**CP<sub>U</sub>** Count Up Clock Pulse Input  
**CP<sub>D</sub>** Count Down Clock Pulse Input  
**MR** Asynchronous Master Reset (Clear) Input  
**PL** Asynchronous Parallel Load (Active LOW) Input  
**P<sub>n</sub>** Parallel Data Inputs  
**Q<sub>n</sub>** Flip-Flop Outputs (Note b)  
**TCD** Terminal Count Down (Borrow) Output (Note b)  
**TCU** Terminal Count Up (Carry) Output (Note b)

NOTES:


a. 1 TTL Unit Load (U.L.) = 40  $\mu$ A HIGH/1.6 mA LOW.

b. The Output LOW drive

 


 
# Pastilhas comerciais:

- Contador síncrono decimal up/down: 74HC160



  
# Pastilhas comerciais:

- Contador síncrono decimal up/down: 74HC160




 
# Pastilhas comerciais:

- Contador síncrono binario up/down: 74HC163



  
# Pastilhas comerciais:


- Contador síncrono binario up/down: 74HC163




# Problema

 

O que faz o circuito abaixo?

 



# Problema

 

**Breve descrição de funcionamento:**

1) O circuito formado pelo Resistor e Capacitor gera um pulso que inicia e continua em nível lógico baixo na saída das portas Schmidt trigger enquanto o capacitor carrega. Chamaremos a este pulso de  $\overline{\text{INIT}}$ . Notar que capacitor carrega rápido, então o sinal  $\overline{\text{INIT}}$  é curto. Uma vez carregado,  $\overline{\text{INIT}}$  permanece em nível lógico alto.

# Problema

 
 


Breve descrição de funcionamento:

2) O sinal  $\overline{\text{INIT}}$  se conecta a 2 pastilhas: a entrada  $\overline{\text{PL}}$  do 74190 e a entrada  $\overline{\text{S}}_d$  do FF-JK. Ambas são assíncronas (não dependem do sinal do clock). Isto força respectivamente o "Parallel Load" do contador com o número  $D_3D_2D_1D_0=0101_{(2)}=5_{(10)}$  e o "Set" do FF-JK. Desta forma, isto garante que o contador inicie a contagem no número 5. Note que saída do FF-JK controla o sentido de contagem do contador. Como neste caso o FF é setado,  $Q=1$ , a entrada  $\overline{\text{U}}/\text{D}=1$ , forçando o contado num contagem decrescente (Down), tão logo o pulso  $\overline{\text{INIT}}$  cesse.

Transição BAIXO para ALTO quando recém alimentado


# Problema

  

Breve descrição de funcionamento:

3) Depois que  $IN\bar{I}T=1$ , e como a entrada  $\bar{C}E$  (Count Enable) está permanente ativada ( $=0$ ), o contador começa a contar, de maneira decrescente (a) já que  $\bar{U}/D=1$  (o FF-JK está setado). Esta condição de contagem continua até o contador atingir o final de contagem, indicado por um novo pulso na saída  $TC$  (b).

# Problema


 


Breve descrição de funcionamento:

4) Quando atinge o final da contagem (número 0), TC, que estava em nível lógico BAIXO, comuta para nível lógico ALTO, esta transição gera impactos no circuito. Note que TC está conectado à entrada de Clock (borda de subida) do FF-JK (que está na configuração toggle). Quando o contador vai reciclar (baixa TC de nível lógico ALTO para BAIXO), a porta NOT na entrada de Clock do JK, faz gerar uma borda de subida no JK, o que por sua vez (dada a configuração toggle do JK), faz alternar sua saída Q de 1 para 0, e assim a contagem passar agora à ser crescente, já que  $\bar{U}/D$  passa para nível lógico BAIXO ( $\bar{U}_p$ ).




# Problema

  

Breve descrição de funcionamento:


5) Anteriormente, o pulso gerado por TC, fez comutar o contador de contagem decrescente para crescente enquanto  $\bar{U}/D$  permanecer em nível lógico BAIXO e assim o contador passa a contar agora até 0 até o número 9 (crescente). Quando atingir o número 9 (final da contagem no modo crescente), note que um novo pulso é gerado na saída TC.

# Problema

 


Breve descrição de funcionamento:

 6) Novamente, a mudança de nível lógico na saída TC do Contador (quando atinge o número 9 e vai para o zero; o "recycle"), através da porta NOT na entrada do FF-JK (que está em configuração toggle) faz alternar a saída do mesmo de 0 para 1, e assim, na próxima borda de subida do sinal de Clock, o Contador vai realizar contagem decrescente (já que agora  $\bar{U}/D$  está em 1).




# Problema

 


Breve descrição de funcionamento:

 
7) Agora, enquanto  $\bar{U}/D$  permanecer em nível lógico ALTO, este contador vai realizar contagem decrescente de 9 até 0. E quando atingir o 0 (final da contagem), o novo pulso gerado na saída TC vai fazer com que o Contador alterne novamente a contagem de decrescente à crescente. E assim o ciclo de contagem segue indefinidamente alternando contagens decrescentes com crescentes enquanto o circuito permanecer alimentado.



# Problema

 

 Em resumo este circuito realiza a seguinte seqüência de contagem:



# Projetos:

- Exemplo: contador síncrono decimal:

 
 


Tabela de transições do FF-JK:

Q(t)	Q(t+1)	J(t)	K(t)
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

# Projetos:

- Exemplo: contador síncrono decimal:

2. Mapas de Karnaugh → Circuito final

$q(t) \rightarrow Q(t+1)$

\* Programação nos FFs

Ref	$q_3 q_2 q_1 q_0$	$Q_3 Q_2 Q_1 Q_0$	$J_3 K_3$	$J_2 K_2$	$J_1 K_1$	$J_0 K_0$
0	0 0 0 0	0 0 0 1	0 X	0 X	0 X	1 X
1	0 0 0 1	0 0 1 0	0 X	0 X	1 X	X 1
2	0 0 1 0	0 0 1 1	0 X	0 X	X 0	1 X
3	0 0 1 1	0 1 0 0	0 X	1 X	X 1	X 1
4	0 1 0 0	0 1 0 1	0 X	X 0	0 X	1 X
5	0 1 0 1	0 1 1 0	0 X	X 0	1 X	X 1
6	0 1 1 0	0 1 1 1	0 X	X 0	X 0	1 X
7	0 1 1 1	1 0 0 0	1 X	X 1	X 1	X 1
8	1 0 0 0	1 0 0 1	X 0	0 X	0 X	1 X
9	1 0 0 1	0 0 0 0 *	X 1	0 X	0 X	X 1
10	1 0 1 0	X X X X	X X	X X	X X	X X
11	1 0 1 1	X X X X	X X	X X	X X	X X
12	1 1 0 0	X X X X	X X	X X	X X	X X
13	1 1 0 1	X X X X	X X	X X	X X	X X
14	1 1 1 0	X X X X	X X	X X	X X	X X
15	1 1 1 1	X X X X	X X	X X	X X	X X

\* Recycle  
 Entrada  
 ↓  
 estado  
 atual

$J_0=1$   $K_0=1$   
 FF está em  
 configuração toggle.

Tabela de transições do FF-JK:

Q(t)	Q(t+1)	J(t)	K(t)
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

# Projetos:

## Exemplo: contador síncrono decimal:


### 1. Tabela de transição de contagem (circuito completo)

$q(t) \rightarrow Q(t+1)$  • Programação dos FFs

Ref	$q_3 q_2 q_1 q_0$	$Q_3 Q_2 Q_1 Q_0$	$J_3 K_3$	$J_2 K_2$	$J_1 K_1$	$J_0 K_0$
0	0000	0001	0 X	0 X	0 X	1 X
1	0001	0010	0 X	0 X	1 X	X 1
2	0010	0011	0 X	0 X	X 0	1 X
3	0011	0100	0 X	1 X	X 1	X 1
4	0100	0101	0 X	X 0	0 X	1 X
5	0101	0110	0 X	X 0	1 X	X 1
6	0110	0111	0 X	X 0	X 0	1 X
7	0111	1000	1 X	X 1	X 1	X 1
8	1000	1001	X 0	0 X	0 X	1 X
9	1001	0000*	X 1	0 X	0 X	X 1
10	1010	X X X X	X X	X X	X X	X X
11	1011	X X X X	X X	X X	X X	X X
12	1100	X X X X	X X	X X	X X	X X
13	1101	X X X X	X X	X X	X X	X X
14	1110	X X X X	X X	X X	X X	X X
15	1111	X X X X	X X	X X	X X	X X

\* Recycle  
 Entrada  
 ↓  
 estado  
 atual

 $J_3=1$   $K_3=1$   
 FF está em  
 configuração toggle.



$\Rightarrow 4 \text{ HC190} \Rightarrow J_3 = K_3 = q_2 \cdot q_1 \cdot q_0 + q_3 \cdot q_0$

# Projetos:





## Exemplo: contador síncrono decimal:

### 1. Tabela de transição de contagem (circuito completo)




$q(t) \rightarrow Q(t+1)$

\* Programação dos FFs

Ref	$q_3 q_2 q_1 q_0$	$Q_3 Q_2 Q_1 Q_0$	$J_3 K_3$	$J_2 K_2$	$J_1 K_1$	$J_0 K_0$
0	0000	0001	0X	0X	0X	1X
1	0001	0010	0X	0X	1X	X1
2	0010	0011	0X	0X	X0	1X
3	0011	0100	0X	1X	X1	X1
4	0100	0101	0X	X0	0X	1X
5	0101	0110	0X	X0	1X	X1
6	0110	0111	0X	X0	X0	1X
7	0111	1000	1X	X1	X1	X1
8	1000	1001	X0	0X	0X	1X
9	1001	1010	X0	0X	0X	X1

    

   $\Rightarrow 4 \text{ HC190} \Rightarrow J_3 = K_3 = q_2 \cdot q_1 \cdot q_0 + q_3 \cdot q_0$




\* Re

DECADE COUNTER LS190

VCC = PIN 16  
GND = PIN 8  
PIN NUMBERS

# Outros projetos:

- Exemplo<sub>2</sub>:

 

opções  $\rightarrow$  FF's - JK  $\Rightarrow$  3 x FF's  $\Rightarrow$  3 x 2 entradas (J, K)  $\Rightarrow$  6 Mapas K  
 $\searrow$  FF's - D  $\Rightarrow$  3 x FF's  $\Rightarrow$  3 x 1 entrada (D)  $\Rightarrow$  3 Mapas K  $\leftarrow$

# Outros projetos:

## Exemplo<sub>2</sub>:

 


Tabela de transição do circuito completo:

Ref	M	$q_2$	$q_1$	$q_0$	$Q_2$	$Q_1$	$Q_0$	$D_2$	$D_1$	$D_0$
0	0	0	0	0	0	1	0	0	1	0
1	0	0	0	1	0	0	0	0	0	0
2	0	0	1	0	1	0	0	1	0	0
3	0	0	1	1	0	0	1	0	0	1
4	0	1	0	0	1	1	0	1	1	0
5	0	1	0	1	0	1	1	0	1	1
6	0	1	1	0	0	0	0	0	0	0
7	0	1	1	1	X	X	X	X	X	X
8	1	0	0	0	0	0	1	0	0	1
9	1	0	0	1	0	1	1	0	1	1
10	1	0	1	0	0	0	0	0	0	0
11	1	0	1	1	1	0	1	1	0	1
12	1	1	0	0	0	1	0	0	1	0
13	1	1	0	1	0	0	0	0	0	0
14	1	1	1	0	1	0	0	1	0	0
15	1	1	1	1	X	X	X	X	X	X




Opções  $\rightarrow$  FF's - JK  $\Rightarrow$  3 x FF's  $\Rightarrow$  3 x 2 entradas (J, K)  $\Rightarrow$  6 Mapas K  
 $\rightarrow$  FF's - D  $\Rightarrow$  3 x FF's  $\Rightarrow$  3 x 1 entrada (D)  $\Rightarrow$  3 Mapas K  $\leftarrow$

# Outros projetos:

## • Exemplo<sub>2</sub>:

Tabola de transição do circuito completo:

Ref	M	q(t)			Q(t+1)			D <sub>2</sub>	D <sub>1</sub>	D <sub>0</sub>
		q <sub>2</sub>	q <sub>1</sub>	q <sub>0</sub>	Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>			
0	0	0	0	0	0	1	0	0	1	0
1	0	0	0	1	0	0	0	0	0	0
2	0	0	1	0	1	0	0	1	0	0
3	0	0	1	1	0	0	1	0	0	1
4	0	1	0	0	1	1	0	1	1	0
5	0	1	0	1	0	1	1	0	1	1
6	0	1	1	0	0	0	0	0	0	0
7	0	1	1	1	X	X	X	X	X	X
8	1	0	0	0	0	0	1	0	0	1
9	1	0	0	1	0	1	1	0	1	1
10	1	0	1	0	0	0	0	0	0	0
11	1	0	1	1	1	0	1	1	0	1
12	1	1	0	0	0	1	0	0	1	0
13	1	1	0	1	0	0	0	0	0	0
14	1	1	1	0	1	0	0	1	0	0
15	1	1	1	1	X	X	X	X	X	X

   

$$\begin{aligned}
 D_2 &= \overline{M} \cdot q_2 \cdot \overline{q_1} \cdot \overline{q_0} + \overline{M} \cdot \overline{q_2} \cdot q_2 \cdot \overline{q_0} + \\
 &\quad + M \cdot q_2 \cdot q_1 + M \cdot q_1 \cdot q_0 \\
 &= \overline{M} \cdot \overline{q_0} (q_2 \cdot \overline{q_1} + \overline{q_2} \cdot q_1) + M \cdot q_1 (q_2 + q_0) \\
 &= \overline{M} \cdot \overline{q_0} (q_2 \odot q_1) + M \cdot q_1 \cdot (q_2 + q_0)
 \end{aligned}$$

$$\begin{aligned}
 D_1 &= \overline{M} \cdot \overline{q_1} \cdot \overline{q_0} + q_2 \cdot \overline{q_1} \cdot \overline{q_0} + \overline{M} \cdot q_2 \cdot q_0 + \\
 &\quad + M \cdot \overline{q_2} \cdot \overline{q_1} \cdot q_0 \\
 &= \overline{q_1} \cdot \overline{q_0} (\overline{M} + q_2) + q_0 (\overline{M} \cdot q_2 + M \cdot \overline{q_2} \cdot \overline{q_1})
 \end{aligned}$$




$$D_0 = q_1 \cdot q_0 + \overline{M} \cdot q_2 \cdot q_0 + M \cdot \overline{q_2} \cdot \overline{q_1}$$

# Outros projetos:

## • Exemplo<sub>2</sub>:

Tabola de transição do circuito completo:

Ref	M	q(t)			Q(t+1)			D <sub>2</sub>	D <sub>1</sub>	D <sub>0</sub>
		q <sub>2</sub>	q <sub>1</sub>	q <sub>0</sub>	Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>			
0	0	0	0	0	0	1	0	0	1	0
1	0	0	0	1	0	0	0	0	0	0
2	0	0	1	0	1	0	0	1	0	0
3	0	0	1	1	0	0	1	0	0	1
4	0	1	0	0	1	1	0	1	1	0
5	0	1	0	1	0	1	1	0	1	1
6	0	1	1	0	0	0	0	0	0	0
7	0	1	1	1	X	X	X	X	X	X
8	1	0	0	0	0	0	1	0	0	1
9	1	0	0	1	0	1	1	0	1	1
10	1	0	1	0	0	0	0	0	0	0
11	1	0	1	1	1	0	1	1	0	1
12	1	1	0	0	0	1	0	0	1	0
13	1	1	0	1	0	0	0	0	0	0
14	1	1	1	0	1	0	0	1	0	0
15	1	1	1	1	X	X	X	X	X	X

   

$$\begin{aligned}
 D_2 &= \bar{M} \cdot q_2 \cdot \bar{q}_1 \cdot \bar{q}_0 + \bar{M} \cdot \bar{q}_2 \cdot q_2 \cdot \bar{q}_0 + \\
 &+ M \cdot q_2 \cdot q_1 + M \cdot q_1 \cdot q_0 \\
 &= \bar{M} \cdot \bar{q}_0 (q_2 \cdot \bar{q}_1 + \bar{q}_2 \cdot q_1) + M \cdot q_1 (q_2 + q_0) \\
 &= \bar{M} \cdot \bar{q}_0 (q_2 \odot q_1) + M \cdot q_1 \cdot (q_2 + q_0)
 \end{aligned}$$




$$\begin{aligned}
 D_1 &= \bar{M} \cdot \bar{q}_1 \cdot \bar{q}_0 + q_2 \cdot \bar{q}_1 \cdot \bar{q}_0 + \bar{M} \cdot q_2 \cdot q_0 + \\
 &+ M \cdot \bar{q}_2 \cdot \bar{q}_1 \cdot q_0 \\
 &= \bar{q}_1 \cdot \bar{q}_0 (\bar{M} + q_2) + q_0 (\bar{M} \cdot q_2 + M \cdot \bar{q}_2 \cdot \bar{q}_1)
 \end{aligned}$$

$$D_0 = q_1 \cdot q_0 + \bar{M} \cdot q_2 \cdot q_0 + M \cdot \bar{q}_2 \cdot \bar{q}_1$$


Outra solução + simples p/circuito?

# Outros projetos:

- Exemplo<sub>2</sub>:

   


 
Outra solução + simples p/ circuito? **Uso de MUXes**



# Outros projetos:

  - Exemplo<sub>2</sub>:




Outra solução + simples p/ circuito? **Uso de MUXes e CI com 4 FF's-D: 74LS175**



# Outros projetos:

   
## ● Exemplo<sub>2</sub>:

Solução + simples p/circuito: **Uso de MUXes e CI com 4 FF's-D: 74LS175**


 
# Detalhe última solução ➡ FPGAs


- Estrutura interna (genérica/simplificada) de um FPGA:



- Este tipo de pastilha permite programar o acionamento de Flip-Flop's através de "lookup tables". A lógica combinacional definida para acinar a(s) entrada(s) de controle do FF fica programada dentro de uma "lookup table", ou "LUT".
- Note a presença de um FF tipo D, um somador completo (FA = Full Adder) e 2 conjuntos de LUT para até 3 variáveis de entrada.
- Note que é comum que o circuito lógico correspondente a cada LUT seja formado usando um Multiplexador, no caso da figura mostrada, seria um MUX para até 8 linhas de entrada, os pontos a, b e c correspondem aos pinos de Select do MUX.
 
# Detalhe última solução ➡ FPGAs




- Estrutura interna (genérica/simplificada) de um FPGA:



- Alguns FPGAs não incluem na sua célula básica um somador completo.
- Neste caso, a saída do MUX é normalmente conectada à entrada de uma porta AND de 2 entradas, onde a segunda entrada da porta AND ficaria conectada ao ponto d (da figura). Note que este ponto d permite que o mesmo atue como um sinal de Enable.
- Uma pastilha FPGA é formada por centenas ou milhares destas células lógicas básicas. Cada célula lógica pode ser conectada a outras células através de recursos de interconexão ("fusíveis") programados por software. Cada célula isoladamente pode fazer pouco, mas com muitas delas conectados juntas, funções lógicas complexas podem ser criadas através de células de Entrada/Saída (IO-cells).
   
# Detalhe última solução ➡ FPGAs


- Estrutura interna (genérica/simplificada) de um FPGA:





Uma pastilha FPGA é formada por centenas ou milhares destas células lógicas básicas. Cada célula lógica pode ser conectada a outras células através de recursos de interconexão ("fusíveis") programados por software. Cada célula isoladamente pode fazer pouco, mas com muitas delas conectados juntas, funções lógicas complexas podem ser criadas através de células de Entrada/Saída (IO-cells).

# Outros projetos:

- Exemplo<sub>3</sub>:

 


Legend:

  


# Outros projetos:

## • Exemplo<sub>3</sub>:

 

Legenda:

- Mode = 0
- Mode = 1

 


Ref	(M) Mode	$q(t)$			$\rightarrow Q(t+1)$			$D_2 D_1 D_0$		
		$q_2$	$q_1$	$q_0$	$Q_2$	$Q_1$	$Q_0$	$D_2$	$D_1$	$D_0$
0	0	0	0	0	0	0	1	0	0	1
1	0	0	0	1	0	1	0	0	1	0
2	0	0	1	0	0	1	1	0	1	1
3	0	0	1	1	1	0	0	1	0	0
4	0	1	0	0	0	0	1	0	0	1
5	0	1	0	1	1	0	0	1	0	0
6	0	1	1	0	1	0	1	1	0	1
7	0	1	1	1	X	X	X	X	X	X
8	1	0	0	0	1	0	0	1	0	0
9	1	0	0	1	1	0	0	1	0	0
10	1	0	1	0	0	0	1	0	0	1
11	1	0	1	1	0	1	0	0	1	0
12	1	1	0	0	1	0	1	1	0	1
13	1	1	0	1	1	1	0	1	1	0
14	1	1	1	0	0	0	0	0	0	0
15	1	1	1	1	X	X	X	X	X	X

# Outros projetos:


## • Exemplo<sub>3</sub>:

Ref	(M) Mode	q(t)			→ Q(t+1)			D <sub>2</sub>	D <sub>1</sub>	D <sub>0</sub>
		q <sub>2</sub>	q <sub>1</sub>	q <sub>0</sub>	Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>			
0	0	0	0	0	0	0	1	0	0	1
1	0	0	0	1	0	1	0	0	1	0
2	0	0	1	0	0	1	1	0	1	1
3	0	0	1	1	1	0	0	1	0	0
4	0	1	0	0	0	0	1	0	0	1
5	0	1	0	1	1	0	0	1	0	0
6	0	1	1	0	1	0	1	1	0	1
7	0	1	1	1	X	X	X	X	X	X
8	1	0	0	0	1	0	0	1	0	0
9	1	0	0	1	1	0	0	1	0	0
10	1	0	1	0	0	0	1	0	0	1
11	1	0	1	1	0	1	0	0	1	0
12	1	1	0	0	1	0	1	1	0	1
13	1	1	0	1	1	1	0	1	1	0
14	1	1	1	0	0	0	0	0	0	0
15	1	1	1	1	X	X	X	X	X	X

D<sub>2</sub>:

 

 
$$D_2 = M \cdot \bar{q}_1 + \bar{M} \cdot q_2 \cdot \bar{q}_0 + \bar{M} \cdot q_1 \cdot q_0 + \bar{M} \cdot q_2 \cdot q_1$$




$$D_1 = \bar{M} \cdot \bar{q}_2 \cdot \bar{q}_1 \cdot q_0 + \bar{M} \cdot \bar{q}_2 \cdot q_1 \cdot \bar{q}_0 + M \cdot q_2 \cdot q_0 + M \cdot q_1 \cdot q_0$$
 
$$= \bar{M} \cdot \bar{q}_2 (q_2 \oplus q_0)$$



$$D_0 = \bar{M} \cdot \bar{q}_0 + \bar{q}_2 \cdot q_1 \cdot \bar{q}_0 + q_2 \cdot \bar{q}_1 \cdot \bar{q}_0$$


# Outros projetos:

 

⇒

M	$q_2 q_1 q_0$	→	$Q_2 Q_1 Q_0$	→	$Q_2 Q_1 Q_0$
0	1 1 1	→	?	→	1 0 0
1	1 1 1	→	?	→	0 1 0

## • Exemplo<sub>3</sub>:

 

Legenda:

- Mode = 0
- Mode = 1

$$D_2 = M \cdot \bar{q}_1 + \bar{M} \cdot q_2 \cdot q_0 + \bar{M} \cdot q_1 \cdot q_0 + \bar{M} \cdot q_2 \cdot q_1$$

$$\text{Mode}=0 \rightarrow D_2 = 0 \cdot \bar{q}_1 + 1 \cdot 1 \cdot 1 + \dots = 1$$

$$\text{Mode}=1 \rightarrow D_2 = 1 \cdot 0 + 0 \cdot q_2 \cdot q_0 + 0 \cdot q_1 \cdot q_0 + 0 \cdot q_2 \cdot q_1 = 0$$

$$D_4 = \bar{M} \cdot \bar{q}_2 \cdot \bar{q}_1 \cdot q_0 + \bar{M} \cdot \bar{q}_2 \cdot q_1 \cdot \bar{q}_0 + M \cdot q_2 \cdot q_0 + M \cdot q_1 \cdot q_0$$


$$\text{Mode}=0 \rightarrow D_4 = \underbrace{1 \cdot \bar{1} \cdot \bar{1} \cdot 1}_0 + \underbrace{1 \cdot \bar{1} \cdot 1 \cdot \bar{1}}_0 + \underbrace{0 \cdot q_2 \cdot q_0}_0 + \underbrace{0 \cdot q_1 \cdot q_0}_0 = 0$$

$$\text{Mode}=1 \rightarrow D_4 = \underbrace{0 \cdot \bar{q}_2 \cdot \bar{q}_1 \cdot q_0}_0 + \underbrace{0 \cdot \bar{q}_2 \cdot q_1 \cdot \bar{q}_0}_0 + \underbrace{1 \cdot 1 \cdot 1}_1 + \dots = 1$$


$$D_0 = \bar{M} \cdot \bar{q}_0 + \bar{q}_2 \cdot q_1 \cdot \bar{q}_0 + q_2 \cdot q_1 \cdot \bar{q}_0$$

$$M=0 \rightarrow D_0 = 1 \cdot 0 + \underbrace{0 \cdot q_1 \cdot \bar{q}_0}_0 + \underbrace{q_2 \cdot q_1 \cdot 0}_0 = 0$$

 
$$M=1 \rightarrow D_0 = 0 \cdot \bar{q}_0 + \underbrace{0 \cdot q_1 \cdot \bar{q}_0}_0 + \underbrace{q_2 \cdot q_1 \cdot 0}_0 = 0$$



Legenda:  
— Mode = 0  
— Mode = 1

 

Legenda:  
— Mode = 0  
— Mode = 1

 

M	q <sub>2</sub>	q <sub>1</sub>	q <sub>0</sub>	→	Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>	→	Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>
0	1	1	1	→	?	?	?	→	1	0	0
1	1	1	1	→	?	?	?	→	0	1	0

7 → Mode 0 → 100<sub>(2)</sub> =

4<sub>(10)</sub>

7 → Mode 1 → 010<sub>(2)</sub> =

2<sub>(10)</sub>

$$D_2 = M \cdot \bar{q}_1 + \bar{M} \cdot q_2 \cdot q_0 + \bar{M} \cdot q_1 \cdot q_0 + \bar{M} \cdot q_2 \cdot q_1$$

Mode=0 →  $D_2 = 0 \cdot \bar{q}_1 + 1 \cdot 1 \cdot 1 + \dots = 1$

Mode=1 →  $D_2 = 1 \cdot 0 + 0 \cdot q_2 \cdot q_0 + 0 \cdot q_1 \cdot q_0 + 0 \cdot q_2 \cdot q_1 = 0$

$$D_1 = \bar{M} \cdot \bar{q}_2 \cdot \bar{q}_1 \cdot q_0 + \bar{M} \cdot \bar{q}_2 \cdot q_1 \cdot \bar{q}_0 + M \cdot q_2 \cdot q_0 + M \cdot q_1 \cdot q_0$$

Mode=0 →  $D_1 = \underbrace{1 \cdot \bar{1} \cdot \bar{1} \cdot 1}_0 + \underbrace{1 \cdot \bar{1} \cdot 1 \cdot \bar{1}}_0 + \underbrace{0 \cdot q_2 \cdot q_0}_0 + \underbrace{0 \cdot q_1 \cdot q_0}_0 = 0$

Mode=1 →  $D_1 = \underbrace{0 \cdot \bar{q}_2 \cdot \bar{q}_1 \cdot q_0}_0 + \underbrace{0 \cdot \bar{q}_2 \cdot q_1 \cdot \bar{q}_0}_0 + \underbrace{1 \cdot 1 \cdot 1}_1 + \dots = 1$


$$D_0 = \bar{M} \cdot \bar{q}_0 + \bar{q}_2 \cdot q_1 \cdot \bar{q}_0 + q_2 \cdot q_1 \cdot \bar{q}_0$$

M=0 →  $D_0 = 1 \cdot 0 + \underbrace{0 \cdot q_1 \cdot \bar{q}_0}_0 + \underbrace{q_2 \cdot q_1 \cdot 0}_0 = 0$

M=1 →  $D_0 = 0 \cdot \bar{q}_0 + \underbrace{0 \cdot q_1 \cdot \bar{q}_0}_0 + \underbrace{q_2 \cdot q_1 \cdot 0}_0 = 0$

# Outros projetos:


## Exemplo<sub>3</sub>:

 

Ref.	(M) Mode	$q(k)$ $q_2 q_1 q_0$	$Q(k+1)$ $Q_2 Q_1 Q_0$	$D_2 D_1 D_0$
0	0	0 0 0	0 0 1	0 0 1
1	0	0 0 1	0 1 0	0 1 0
2	0	0 1 0	0 1 1	0 1 1
3	0	0 1 1	1 0 0	1 0 0
4	0	1 0 0	0 0 1	0 0 1
5	0	1 0 1	1 0 0	1 0 0
6	0	1 1 0	1 0 1	1 0 1
7	0	1 1 1	X X X	X X X
8	1	0 0 0	1 0 0	1 0 0
9	1	0 0 1	1 0 0	1 0 0
10	1	0 1 0	0 0 1	0 0 1
11	1	0 1 1	0 1 0	0 1 0
12	1	1 0 0	1 0 1	1 0 1
13	1	1 0 1	1 1 0	1 1 0
14	1	1 1 0	0 0 0	0 0 0
15	1	1 1 1	X X X	X X X


Outra solução + simples p/ circuito?

$D_2$ :

 


$$D_2 = M \cdot \bar{q}_1 + \bar{M} \cdot q_2 \cdot \bar{q}_0 + \bar{M} \cdot q_1 \cdot q_0 + \bar{M} \cdot q_2 \cdot q_1 \cdot q_0$$

$D_1$ :

 

$D_0$ :

 

$$D_0 = \bar{M} \cdot \bar{q}_0 + q_2 \cdot q_1 \cdot \bar{q}_0 + q_2 \cdot \bar{q}_1 \cdot \bar{q}_0$$


$$D_2 = \bar{M} \cdot \bar{q}_2 \cdot \bar{q}_1 \cdot q_0 + \bar{M} \cdot \bar{q}_2 \cdot q_1 \cdot \bar{q}_0 + M \cdot q_2 \cdot \bar{q}_0 + M \cdot q_1 \cdot q_0$$

$$M \cdot \bar{q}_2 (q_2 \oplus q_0)$$

# Outros projetos:


## ● Exemplo<sub>3</sub>:

Outra solução + simples: Uso de MUXes:

 

Ref	(M) Mode	q(k)			→ Q(k+1)			D <sub>2</sub> D <sub>1</sub> D <sub>0</sub>		
		q <sub>2</sub>	q <sub>1</sub>	q <sub>0</sub>	Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>	D <sub>2</sub>	D <sub>1</sub>	D <sub>0</sub>
0	0	0	0	0	0	0	1	0	0	1
1	0	0	0	1	0	1	0	0	1	0
2	0	0	1	0	0	1	1	0	1	1
3	0	0	1	1	1	0	0	1	0	0
4	0	1	0	0	0	0	1	0	0	1
5	0	1	0	1	1	0	0	1	0	0
6	0	1	1	0	1	0	1	1	0	1
7	0	1	1	1	X	X	X	X	X	X
8	1	0	0	0	1	0	0	1	0	0
9	1	0	0	1	1	0	0	1	0	0
10	2	0	1	0	0	0	1	0	0	1
11	1	0	1	1	0	1	0	0	1	0
12	1	1	0	0	1	0	1	1	0	1
13	1	1	0	1	1	1	0	1	1	0
14	1	1	1	0	0	0	0	0	0	0
15	1	1	1	1	X	X	X	X	X	X


Ref'	Ref	M	q <sub>2</sub>	q <sub>1</sub>	q <sub>0</sub>	D <sub>2</sub>
0	0	0	0	0	0	0
1	1	0	0	0	1	0
2	2	0	0	1	0	0
3	3	0	0	1	1	1
4	4	0	1	0	0	0
5	5	0	1	0	1	1
6	6	0	1	1	0	1
7	7	0	1	1	1	0
8	8	1	0	0	0	1
9	9	1	0	0	1	1
10	10	1	0	1	0	0
11	11	1	0	1	1	0
12	12	1	1	0	0	1
13	13	1	1	0	1	1
14	14	1	1	1	0	0
15	15	1	1	1	1	0

 

# Outros projetos:


## ● Exemplo<sub>3</sub>:

Outra solução + simples: Uso de MUXes:

 

Ref	(M) Mode	q(k)			→ Q(k+1)			D <sub>2</sub>	D <sub>1</sub>	D <sub>0</sub>
		q <sub>2</sub>	q <sub>1</sub>	q <sub>0</sub>	q <sub>2</sub>	q <sub>1</sub>	q <sub>0</sub>			
0	0	0	0	0	0	0	1	0	0	1
1	0	0	0	1	0	1	0	0	1	0
2	0	0	1	0	0	1	1	0	1	1
3	0	0	1	1	1	0	0	1	0	0
4	0	1	0	0	0	0	1	0	0	1
5	0	1	0	1	1	0	0	1	0	0
6	0	1	1	0	1	0	1	1	0	1
7	0	1	1	1	X	X	X	X	X	X
8	1	0	0	0	1	0	0	1	0	0
9	1	0	0	1	1	0	0	1	0	0
10	1	0	1	0	0	0	1	0	0	1
11	1	0	1	1	0	1	0	0	1	0
12	1	1	0	0	1	0	1	1	0	1
13	1	1	0	1	1	1	0	1	1	0
14	1	1	1	0	0	0	0	0	0	0
15	1	1	1	1	X	X	X	X	X	X


Ref <sup>1</sup>	Ref	M	q <sub>2</sub>	q <sub>1</sub>	q <sub>0</sub>	D <sub>1</sub>
0	0	0	0	0	0	0
1	1	0	0	0	1	1
2	2	0	0	1	0	1
3	3	0	0	1	1	0
4	4	0	1	0	0	0
5	5	0	1	0	1	0
6	6	0	1	1	0	0
7	7	0	1	1	1	0
8	8	1	0	0	0	0
9	9	1	0	0	1	0
10	10	1	0	1	0	0
11	11	1	0	1	1	1
12	12	1	1	0	0	0
13	13	1	1	0	1	1
14	14	1	1	1	0	0
15	15	1	1	1	1	0

 

# Outros projetos:

## ● Exemplo<sub>3</sub>:

Outra solução + simples: Uso de MUXes:

 

Ref	(M) Mode	q(k)			→ Q(k+1)			D <sub>2</sub>	D <sub>1</sub>	D <sub>0</sub>
		q <sub>2</sub>	q <sub>1</sub>	q <sub>0</sub>	Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>			
0	0	0	0	0	0	0	1	0	0	1
1	0	0	0	1	0	1	0	0	1	0
2	0	0	1	0	0	1	1	0	1	1
3	0	0	1	1	1	0	0	1	0	0
4	0	1	0	0	0	0	1	0	0	1
5	0	1	0	1	1	0	0	1	0	0
6	0	1	1	0	1	0	1	1	0	1
7	0	1	1	1	X	X	X	X	X	X
8	1	0	0	0	1	0	0	1	0	0
9	1	0	0	1	1	0	0	1	0	0
10	2	0	1	0	0	0	1	0	0	1
11	1	0	1	1	0	1	0	0	1	0
12	1	1	0	0	1	0	1	1	0	1
13	1	1	0	1	1	1	0	1	1	0
14	1	1	1	0	0	0	0	0	0	0
15	1	1	1	1	X	X	X	X	X	X

Ref'	Ref	M	q <sub>2</sub>	q <sub>1</sub>	q <sub>0</sub>	D <sub>0</sub>
0	0	0	0	0	0	1
1	1	0	0	0	1	0
2	2	0	0	1	0	1
3	3	0	0	1	1	0
4	4	0	1	0	0	1
5	5	0	1	0	1	0
6	6	0	1	1	0	1
7	7	0	1	1	1	0
8	8	1	0	0	0	0
9	9	1	0	0	1	0
10	10	1	0	1	0	1
11	11	1	0	1	1	0
12	12	1	1	0	0	1
13	13	1	1	0	1	0
14	14	1	1	1	0	0
15	15	1	1	1	1	0

$X_0 = \bar{M}$   
 $X_1 = 0$   
 $X_2 = 1$   
 $X_3 = 0$   
 $X_4 = 1$   
 $X_5 = 0$   
 $X_6 = \bar{M}$   
 $X_7 = 0$